

Contents

PREFACE	v		
EQUIPMENT LIST	vii		
EXPERIMENT	1	OSCILLOSCOPE AND FUNCTION GENERATOR OPERATION	1
EXPERIMENT	2	DIODE CHARACTERISTICS	13
EXPERIMENT	3	SERIES AND PARALLEL DIODE CONFIGURATIONS	25
EXPERIMENT	4	HALF-WAVE AND FULL-WAVE RECTIFICATION	37
EXPERIMENT	5	CLIPPING CIRCUITS	53
EXPERIMENT	6	CLAMPING CIRCUITS	67
EXPERIMENT	7	LIGHT-EMITTING AND ZENER DIODES	81
EXPERIMENT	8	BIPOLAR JUNCTION TRANSISTOR (BJT) CHARACTERISTICS	95
EXPERIMENT	9	FIXED- AND VOLTAGE-DIVIDER BIAS OF BJTS	105
EXPERIMENT	10	EMITTER AND COLLECTOR FEEDBACK BIAS OF BJTS	119
EXPERIMENT	11	DESIGN OF BJT BIAS CIRCUITS	139
EXPERIMENT	12	JFET CHARACTERISTICS	159
EXPERIMENT	13	JFET BIAS CIRCUITS	173
EXPERIMENT	14	DESIGN OF JFET BIAS CIRCUITS	187
EXPERIMENT	15	COMPOUND CONFIGURATIONS	203
EXPERIMENT	16	MEASUREMENT TECHNIQUES	221
EXPERIMENT	17	COMMON-EMITTER TRANSISTOR AMPLIFIERS	239
EXPERIMENT	18	COMMON-BASE AND EMITTER-FOLLOWER (COMMON-COLLECTOR) TRANSISTOR AMPLIFIERS	249
EXPERIMENT	19	DESIGN OF COMMON-EMITTER AMPLIFIERS	269
EXPERIMENT	20	COMMON-SOURCE TRANSISTOR AMPLIFIERS	277
EXPERIMENT	21	MULTISTAGE AMPLIFIERS: RC COUPLING	287
EXPERIMENT	22	CMOS CIRCUITS	303
EXPERIMENT	23	DARLINGTON AND CASCODE AMPLIFIER CIRCUITS	309

EXPERIMENT	24	CURRENT SOURCE AND CURRENT MIRROR CIRCUITS	321
EXPERIMENT	25	FREQUENCY RESPONSE OF COMMON-EMITTER AMPLIFIERS	329
EXPERIMENT	26	CLASS-A AND CLASS-B POWER AMPLIFIERS	339
EXPERIMENT	27	DIFFERENTIAL AMPLIFIER CIRCUITS	351
EXPERIMENT	28	OP-AMP CHARACTERISTICS	369
EXPERIMENT	29	LINEAR OP-AMP CIRCUITS	377
EXPERIMENT	30	ACTIVE FILTER CIRCUITS	389
EXPERIMENT	31	COMPARATOR CIRCUITS OPERATION	401
EXPERIMENT	32	OSCILLATOR CIRCUITS 1: THE PHASE-SHIFT OSCILLATOR	411
EXPERIMENT	33	OSCILLATOR CIRCUITS 2	419
EXPERIMENT	34	VOLTAGE REGULATION—POWER SUPPLIES	429
EXPERIMENT	35	ANALYSIS OF AND, NAND, AND INVERTER LOGIC GATES	437
EXPERIMENT	36	ANALYSIS OF OR, NOR, AND XOR LOGIC GATES	447
EXPERIMENT	37	ANALYSIS OF INTEGRATED CIRCUITS	459