

Contents

List of Examples xiii

Preface xvii

Chapter 1 Circuit Variables 2

Practical Perspective: Balancing Power 3

1.1 Electrical Engineering: An Overview 4

1.2 The International System of Units 8

1.3 Circuit Analysis: An Overview 10

1.4 Voltage and Current 11

1.5 The Ideal Basic Circuit Element 12

1.6 Power and Energy 14

Practical Perspective: Balancing Power 17

Summary 18

Problems 19

Chapter 2 Circuit Elements 24

Practical Perspective: Heating with Electric Radiators 25

2.1 Voltage and Current Sources 26

2.2 Electrical Resistance (Ohm's Law) 30

2.3 Construction of a Circuit Model 34

2.4 Kirchhoff's Laws 37

2.5 Analysis of a Circuit Containing Dependent Sources 42

Practical Perspective: Heating with Electric Radiators 46

Summary 48

Problems 48

Chapter 3 Simple Resistive Circuits 56

Practical Perspective: Resistive Touch Screens 57

3.1 Resistors in Series 58

3.2 Resistors in Parallel 59

3.3 The Voltage-Divider and Current-Divider Circuits 61

3.4 Voltage Division and Current Division 64

3.5 Measuring Voltage and Current 66

3.6 Measuring Resistance—The Wheatstone Bridge 69

3.7 Delta-to-Wye (Pi-to-Tee) Equivalent Circuits 71

Practical Perspective: Resistive Touch Screens 73

Summary 75

Problems 76

Chapter 4 Techniques of Circuit Analysis 88

Practical Perspective: Circuits with Realistic Resistors 89

4.1 Terminology 90

4.2 Introduction to the Node-Voltage Method 93

4.3 The Node-Voltage Method and Dependent Sources 95

4.4 The Node-Voltage Method: Some Special Cases 96

4.5 Introduction to the Mesh-Current Method 99

4.6 The Mesh-Current Method and Dependent Sources 102

4.7 The Mesh-Current Method: Some Special Cases 103

4.8 The Node-Voltage Method Versus the Mesh-Current Method 106

4.9 Source Transformations 109

4.10 Thévenin and Norton Equivalents 113

4.11 More on Deriving a Thévenin Equivalent 117

4.12 Maximum Power Transfer 120

4.13 Superposition 122

Practical Perspective: Circuits with Realistic Resistors 125

Summary 129

Problems 130

Chapter 5 The Operational Amplifier 144

Practical Perspective: Strain Gages 145

5.1 Operational Amplifier Terminals 146

5.2 Terminal Voltages and Currents 146

5.3 The Inverting-Amplifier Circuit 150

5.4 The Summing-Amplifier Circuit 152

5.5 The Noninverting-Amplifier Circuit 153

5.6 The Difference-Amplifier Circuit 155

5.7 A More Realistic Model for the Operational Amplifier 159

Practical Perspective: Strain Gages 162

Summary 164

Problems 165

Chapter 6 Inductance, Capacitance, and Mutual Inductance 174

Practical Perspective: Capacitive Touch Screens 175

- 6.1 The Inductor 176
 - 6.2 The Capacitor 182
 - 6.3 Series-Parallel Combinations of Inductance and Capacitance 187
 - 6.4 Mutual Inductance 189
 - 6.5 A Closer Look at Mutual Inductance 193
- Practical Perspective: Capacitive Touch Screens* 200
- Summary* 202
- Problems* 204

Chapter 7 Response of First-Order *RL* and *RC* Circuits 212

Practical Perspective: Artificial Pacemaker 213

- 7.1 The Natural Response of an *RL* Circuit 214
 - 7.2 The Natural Response of an *RC* Circuit 220
 - 7.3 The Step Response of *RL* and *RC* Circuits 224
 - 7.4 A General Solution for Step and Natural Responses 231
 - 7.5 Sequential Switching 236
 - 7.6 Unbounded Response 240
 - 7.7 The Integrating Amplifier 241
- Practical Perspective: Artificial Pacemaker* 245
- Summary* 246
- Problems* 247

Chapter 8 Natural and Step Responses of *RLC* Circuits 264

Practical Perspective: Clock for Computer Timing 265

- 8.1 Introduction to the Natural Response of a Parallel *RLC* Circuit 266
 - 8.2 The Forms of the Natural Response of a Parallel *RLC* Circuit 270
 - 8.3 The Step Response of a Parallel *RLC* Circuit 280
 - 8.4 The Natural and Step Response of a Series *RLC* Circuit 285
 - 8.5 A Circuit with Two Integrating Amplifiers 289
- Practical Perspective: Clock for Computer Timing* 293
- Summary* 295
- Problems* 296

Chapter 9 Sinusoidal Steady-State Analysis 304

Practical Perspective: A Household Distribution Circuit 305

- 9.1 The Sinusoidal Source 306
 - 9.2 The Sinusoidal Response 309
 - 9.3 The Phasor 310
 - 9.4 The Passive Circuit Elements in the Frequency Domain 315
 - 9.5 Kirchhoff's Laws in the Frequency Domain 319
 - 9.6 Series, Parallel, and Delta-to-Wye Simplifications 320
 - 9.7 Source Transformations and Thévenin-Norton Equivalent Circuits 327
 - 9.8 The Node-Voltage Method 330
 - 9.9 The Mesh-Current Method 331
 - 9.10 The Transformer 332
 - 9.11 The Ideal Transformer 336
 - 9.12 Phasor Diagrams 342
- Practical Perspective: A Household Distribution Circuit* 344
- Summary* 345
- Problems* 346

Chapter 10 Sinusoidal Steady-State Power Calculations 358

Practical Perspective: Vampire Power 359

- 10.1 Instantaneous Power 360
 - 10.2 Average and Reactive Power 361
 - 10.3 The rms Value and Power Calculations 366
 - 10.4 Complex Power 368
 - 10.5 Power Calculations 369
 - 10.6 Maximum Power Transfer 376
- Practical Perspective: Vampire Power* 382
- Summary* 384
- Problems* 385

Chapter 11 Balanced Three-Phase Circuits 396

Practical Perspective: Transmission and Distribution of Electric Power 397

- 11.1 Balanced Three-Phase Voltages 398
 - 11.2 Three-Phase Voltage Sources 399
 - 11.3 Analysis of the Wye-Wye Circuit 400
 - 11.4 Analysis of the Wye-Delta Circuit 405
 - 11.5 Power Calculations in Balanced Three-Phase Circuits 408
 - 11.6 Measuring Average Power in Three-Phase Circuits 413
- Practical Perspective: Transmission and Distribution of Electric Power* 416
- Summary* 417
- Problems* 418

Chapter 12 Introduction to the Laplace Transform 426

- Practical Perspective: Transient Effects* 427
- 12.1 Definition of the Laplace Transform 428
- 12.2 The Step Function 429
- 12.3 The Impulse Function 431
- 12.4 Functional Transforms 434
- 12.5 Operational Transforms 435
- 12.6 Applying the Laplace Transform 440
- 12.7 Inverse Transforms 442
- 12.8 Poles and Zeros of $F(s)$ 452
- 12.9 Initial- and Final-Value Theorems 453
- Practical Perspective: Transient Effects* 456
- Summary* 457
- Problems* 458

Chapter 13 The Laplace Transform in Circuit Analysis 464

- Practical Perspective: Surge Suppressors* 465
- 13.1 Circuit Elements in the s Domain 466
- 13.2 Circuit Analysis in the s Domain 468
- 13.3 Applications 470
- 13.4 The Transfer Function 482
- 13.5 The Transfer Function in Partial Fraction Expansions 484
- 13.6 The Transfer Function and the Convolution Integral 487
- 13.7 The Transfer Function and the Steady-State Sinusoidal Response 493
- 13.8 The Impulse Function in Circuit Analysis 496
- Practical Perspective: Surge Suppressors* 503
- Summary* 504
- Problems* 505

Chapter 14 Introduction to Frequency Selective Circuits 520

- Practical Perspective: Pushbutton Telephone Circuits* 521
- 14.1 Some Preliminaries 522
- 14.2 Low-Pass Filters 524
- 14.3 High-Pass Filters 530
- 14.4 Bandpass Filters 534
- 14.5 Bandreject Filters 543
- Practical Perspective: Pushbutton Telephone Circuits* 548
- Summary* 548
- Problems* 549

Chapter 15 Active Filter Circuits 556

- Practical Perspective: Bass Volume Control* 557
- 15.1 First-Order Low-Pass and High-Pass Filters 558
- 15.2 Scaling 562
- 15.3 Op Amp Bandpass and Bandreject Filters 564
- 15.4 Higher Order Op Amp Filters 571
- 15.5 Narrowband Bandpass and Bandreject Filters 584
- Practical Perspective: Bass Volume Control* 589
- Summary* 592
- Problems* 593

Chapter 16 Fourier Series 602

- Practical Perspective: Active High-Q Filters* 603
- 16.1 Fourier Series Analysis: An Overview 605
- 16.2 The Fourier Coefficients 606
- 16.3 The Effect of Symmetry on the Fourier Coefficients 609
- 16.4 An Alternative Trigonometric Form of the Fourier Series 615
- 16.5 An Application 617
- 16.6 Average-Power Calculations with Periodic Functions 621
- 16.7 The rms Value of a Periodic Function 624
- 16.8 The Exponential Form of the Fourier Series 625
- 16.9 Amplitude and Phase Spectra 628
- Practical Perspective: Active High-Q Filters* 630
- Summary* 632
- Problems* 633

Chapter 17 The Fourier Transform 642

- Practical Perspective: Filtering Digital Signals* 643
- 17.1 The Derivation of the Fourier Transform 644
- 17.2 The Convergence of the Fourier Integral 646
- 17.3 Using Laplace Transforms to Find Fourier Transforms 648
- 17.4 Fourier Transforms in the Limit 651
- 17.5 Some Mathematical Properties 653
- 17.6 Operational Transforms 655
- 17.7 Circuit Applications 659
- 17.8 Parseval's Theorem 662
- Practical Perspective: Filtering Digital Signals* 669
- Summary* 670
- Problems* 670

Chapter 18 Two-Port Circuits 676

Practical Perspective: Characterizing an Unknown Circuit 677

- 18.1 The Terminal Equations 678
- 18.2 The Two-Port Parameters 679
- 18.3 Analysis of the Terminated Two-Port Circuit 687
- 18.4 Interconnected Two-Port Circuits 692
 - Practical Perspective: Characterizing an Unknown Circuit 695*
 - Summary 696*
 - Problems 696*

Appendix A The Solution of Linear Simultaneous Equations 703

- A.1 Preliminary Steps 703
- A.2 Cramer's Method 704
- A.3 The Characteristic Determinant 704
- A.4 The Numerator Determinant 704
- A.5 The Evaluation of a Determinant 705
- A.6 Matrices 707
- A.7 Matrix Algebra 708
- A.8 Identity, Adjoint, and Inverse Matrices 712
- A.9 Partitioned Matrices 715
- A.10 Applications 718

Appendix B Complex Numbers 723

- B.1 Notation 723
- B.2 The Graphical Representation of a Complex Number 724
- B.3 Arithmetic Operations 725
- B.4 Useful Identities 726
- B.5 The Integer Power of a Complex Number 727
- B.6 The Roots of a Complex Number 727

Appendix C More on Magnetically Coupled Coils and Ideal Transformers 729

- C.1 Equivalent Circuits for Magnetically Coupled Coils 729
- C.2 The Need for Ideal Transformers in the Equivalent Circuits 733

Appendix D The Decibel 737

Appendix E Bode Diagrams 739

- E.1 Real, First-Order Poles and Zeros 739
- E.2 Straight-Line Amplitude Plots 740
- E.3 More Accurate Amplitude Plots 744
- E.4 Straight-Line Phase Angle Plots 745
- E.5 Bode Diagrams: Complex Poles and Zeros 747
- E.6 Amplitude Plots 749
- E.7 Correcting Straight-Line Amplitude Plots 750
- E.8 Phase Angle Plots 753

Appendix F An Abbreviated Table of Trigonometric Identities 757

Appendix G An Abbreviated Table of Integrals 759

Appendix H Common Standard Component Values 761

Answers to Selected Problems 763

Index 775