
An Introduction to Electronics

William G. Oldham University of California, Berkeley

Steven E. Schwarz University of California, Berkeley

Holt, Rinehart and Winston, Inc.

New York Chicago San Francisco Atlanta
Dallas Montreal Toronto London Sydney

Contents

Preface iii

Foreword What is Electronics? x

1. Principles of Electric Circuits 1

1.1 Information and Signals	1
1.2 Electrical Definitions and Principles	4
1.3 Circuit Elements	17
1.4 Node and Loop Analysis	35
1.5 Voltage and Current Dividers	43
Summary	45
References	46
Problems	46

2. Techniques of Circuit Analysis 53

2.1 Equivalent Circuits	54
2.2 Nonlinear Circuit Elements	68
2.3 Natural Response and Forced Response	74
2.4 Superposition	90
Summary	92
References	93
Problems	94

3. Active Circuits and Building Blocks 99

3.1 Dependent Voltage and Current Sources	101
3.2 Linear Models for Active Devices and Blocks	105
3.3 Building Blocks for Analog Systems	109
3.4 Building Blocks for Digital Systems	114
Summary	124
References	125
Problems	125

4. Sinusoidal Analysis and Phasors 131

4.1 Properties of Sinusoids	132
4.2 Phasors	135
4.3 Impedance	148
4.4 Applications of Sinusoidal Analysis	159
Summary	171
References	172
Problems	173

5. Properties and Applications of Diodes 179

- 5.1 Electrons and Holes 180
- 5.2 *p**n* Junctions 187
- 5.3 The Diode as a Circuit Element 196
- 5.4 Rectifier Circuits 207
- 5.5 Diode Logic Circuits 214
 - Summary 219
 - References 220
 - Problems 221

6. Junction Transistors 227

- 6.1 Transistor Principles 228
- 6.2 Transistor Operation in the Active Mode 233
- 6.3 Large Signal Operation 243
- 6.4 Transistor Characteristics: Comparison with Theory 257
 - Summary 263
 - References 263
 - Problems 264

7. Integrated Circuit Technology 266

- 7.1 Modern Semiconductor Technology 275
- 7.2 Integrated Circuits 292
 - Summary 313
 - References 313
 - Problems 314

6. Introduction to Digital Circuits 317

- 8.1 The Transistor Inverter 318
- 8.2 Diode-Transistor Logic 329
- 8.3 The Flip-Flop 350
 - Summary 354
 - References 355
 - Problems 355

9. Analysis and Synthesis of Digital Systems 359

- 9.1 Switching Algebra 361
- 9.2 Analysis and Synthesis of Combinational Circuits 379
- 9.3 Characteristics of Basic Sequential Circuits 391
- 9.4 Analysis and Synthesis of Flip-Flop Circuits 395
 - Summary 417
 - References 418
 - Problems 418

10. Introduction to Amplifiers 424

- 10.1 Biasing Circuits 428
- 10.2 The Small-Signal Transistor Model 431
- 10.3 Common-Emitter Amplifier Circuits 438
- 10.4 Multistage Common-Emitter Amplifiers 446
- 10.5 Improved Transistor Models 448

10.6 Frequency Response of Amplifier Circuits	451
Summary	462
References	463
Problems	464

11. Design Techniques for Linear Circuits 469

11.1 Differential Amplifiers	473
11.2 Output Circuits	483
11.3 Interstage Coupling	488
11.4 The Complete Amplifier	490
Summary	493
References	494
Problems	495

12. Operational Amplifiers and Their Applications 496

12.1 Characteristics of Operational Amplifiers	502
12.2 Operational Amplifier Circuits	508
12.3 Design Considerations in Op-Amp Circuits	525
Summary	541
References	542
Problems	542

13. MOS Transistors and Integrated Circuits 547

13.1 Characteristics of MOS Transistors	554
13.2 MOS Digital Circuits	563
13.3 MOS Integrated Circuits	584
Summary	588
References	590
Problems	590

Appendix I The Binary Number System 594

Summary	599
References	599
Problems	600

Appendix II An Elementary Theory of *pn* Junctions 602

II.1 Current Flow in Semiconductors	602
II.2 <i>pn</i> Junction Theory	611
Summary	624
References	624
Problems	624