

# CONTENTS

---

<b>Series Preface</b>	<b>vii</b>
<b>Preface</b>	<b>ix</b>
<b>Contributors</b>	<b>xi</b>

## **PART I GENERAL TOPICS**

<b>1. Introduction to the Handbook</b>	<b>1</b>
1.1 Overview	1
1.1.1 Objectives of this Handbook	
1.1.2 Systems Approach	
1.1.3 Impact of the Digital Computer on Instrumentation Systems	
1.1.4 Impact of the Digital Computer on Control Systems	
1.1.5 Organization of this Reference Book	
1.2 General Topics	6
1.3 Instrumentation	6
1.4 Control	7
1.5 Instrumentation and Control Definitions, Terminology, and Concepts	7
1.5.1 Static versus Dynamic Characteristics	
1.5.2 Accuracy and Resolution	
1.5.3 Calibration	
1.5.4 Full-Scale, Range, and Span	
1.5.5 DC and AC	
<b>2. Systems Engineering Concepts</b>	<b>11</b>
2.1 Introduction	11
2.2 Historical Systems Control Highlights	12
2.2.1 Ctesibios (250 B.C.): The Water Clock Regulator	
2.2.2 Cornelis Drebbel (1624): Temperature Control	
2.2.3 Denis Papin (1707): Pressure Regulation	
2.2.4 Edmund Lee (1745): Windpower Control	
2.2.5 James Watt (1789): Steam Engine Speed Regulation	
2.2.6 Charles Babbage (1822): The Analytical Engine	
2.2.7 Macfarlane Gray (1867): Automatic Helmsman	
2.2.8 James Maxwell (1868): Early Control Theory	
2.2.9 Lord Kelvin (1876): The Mechanical Analog Computer	
2.2.10 Elmer Sperry and Sons (1911): The Autopilot	
2.2.11 Vannevar Bush (1927): The Analog Computer	
2.2.12 Alan Turing (1936): Modern Digital Computers	
2.2.13 Black, Nyquist, and Bode (1930s): Theoretical Foundations	
2.2.14 The Modern Era of Theoretical Developments	
2.2.15 Historical Perspective	

vi		CONTENTS	
2.3	Systems Engineering and Control Definitions		20
	2.3.1 Overview 2.3.2 Basic Concepts 2.3.3 Advanced Concepts		
	2.3.4 Control System Elements 2.3.5 Control System Tools		
<b>3.</b>	<b>Dynamic Systems Analysis</b>		<b>27</b>
3.1	Introduction		27
3.2	Physical System Descriptions		27
	3.2.1 General Concepts 3.2.2 Lumped Parameter Element Models		
	3.2.3 General Form of State Equations		
3.3	Linearity and Superposition		34
	3.3.1 Linearization of Nonlinear Equations 3.3.2 Principle of Superposition		
3.4	System Variable Representation and Transformation		36
	3.4.1 Input Variable Characterization 3.4.2 Singularity Functions		
	3.4.3 Fourier Series Representation of Periodic Functions 3.4.4 Fourier Transforms		
	3.4.5 Laplace Transforms 3.4.6 Random Variable Characterization		
3.5	Transfer Function Representation of Linear Systems		43
	3.5.1 Definition 3.5.2 System Transfer Function Synthesis from Operational Block Diagrams		
	3.5.3 Transfer Function Properties 3.5.4 Standard Forms		
3.6	System Transient Response		46
	3.6.1 Solution Techniques 3.6.2 Solutions to First- and Second-Order Systems		
	3.6.3 System Specifications in the Time Domain		
3.7	Frequency Response		51
	3.7.1 Analysis Technique 3.7.2 First- and Second-Order System Frequency Response		
	3.7.3 Generalized Frequency Response Techniques		
	3.7.4 System Specifications in the Frequency Domain		
3.8	System Response to Random Inputs		57
	3.8.1 Basic Relationships 3.8.2 Second-Order System Response		
	3.8.3 Multiple Input System		
<b>4.</b>	<b>Instrument Statics</b>		<b>61</b>
4.1	Terminology		61
	4.1.1 Transducer Characteristics 4.1.2 Definitions		
4.2	Static Calibration		63
	4.2.1 The Calibration Process 4.2.2 Fitting Equations to Calibration Data		
4.3	Statistics in the Measurement Process		67
	4.3.1 Unbiased Estimates 4.3.2 Sampling 4.3.3 Types of Errors		
	4.3.4 Propagation of Error or Uncertainty 4.3.5 Uncertainty Interval		
	4.3.6 Amount of Data to Take 4.3.7 Goodness-of-Fit		
	4.3.8 Probability Density Functions 4.3.9 Determination of Confidence Limits on $\mu$		
	4.3.10 Confidence Limits on Regression Lines		
	4.3.11 Inference and Comparison		

	CONTENTS		vii
<b>5.</b>	<b>Input and Output Characteristics</b>		<b>87</b>
5.1	Introduction		87
5.2	Familiar Examples of Input-Output Interactions		88
	5.2.1 Power Exchange 5.2.2 Energy Exchange 5.2.3 A Human Example		
5.3	Energy, Power, Impedance		90
	5.3.1 Definitions and Analogies 5.3.2 Impedance and Admittance		
	5.3.3 Combining Impedances and/or Admittances 5.3.4 Computing Impedance or Admittance at an Input or Output		
	5.3.5 Transforming or Gyration Impedances 5.3.6 Source Equivalents: Thévenin and Norton		
5.4	The Operating Point of Static Systems		97
	5.4.1 Exchange of Real Power 5.4.2 Operating Points in an Exchange of Power or Energy		
	5.4.3 Input and Output Impedance at the Operating Point 5.4.4 Operating Point and Load for Maximum Transfer of Power		
	5.4.5 An Unstable Energy Exchange: Tension Testing Machine		
	5.4.6 Fatigue in Bolted Assemblies 5.4.7 Operating Point for Nonlinear Characteristics		
	5.4.8 Graphical Determination of Output Impedance for Nonlinear Systems		
5.5	Transforming the Operating Point		107
	5.5.1 Transducer-Matched Impedances 5.5.2 Impedance Requirements for Mixed Systems		
5.6	Measurement Systems		111
	5.6.1 Interaction in Instrument Systems 5.6.2 Dynamic Interactions in Instrument Systems		
	5.6.3 Null Instruments		
5.7	Distributed Systems in Brief		115
	5.7.1 The Impedance of a Distributed System		
5.8	Concluding Remarks		116
<b>6.</b>	<b>Electronic Devices and Data Conversion</b>		<b>117</b>
6.1	Analog Operational Amplifiers		117
	6.1.1 Open-Loop Versus Closed-Loop Behavior 6.1.2 Op Amp Specifications		
	6.1.3 Operational Amplifier Applications 6.1.4 Instrumentation Amplifiers		
6.2	Data Conversion to the Digital Domain		137
	6.2.1 Comparators 6.2.2 Digital Codes 6.2.3 Analog-to-Digital Converters		
6.3	Conversion from the Digital to the Analog Domain		149
	6.3.1 Digital-to-Analog Converters 6.3.2 D/A Converter Specifications and Testing		
	6.3.3 Temperature Effects in Digital-to-Analog Converters		
	6.3.4 IC Technologies for D/A Converter Components 6.3.5 Basic D/A Conversion Techniques		
	6.3.6 Microprocessor Interfacing 6.3.7 CMOS Digital-to-Analog Converters		
6.4	Data Acquisition Subsystems		165
	6.4.1 Sample Theory 6.4.2 Sample/Hold Amplifiers 6.4.3 Multiplexers		

viii		CONTENTS	
6.5	Digital Integrated Circuits		169
	6.5.1 Logic 6.5.2 Boolean Logic Notation 6.5.3 Flip-Flops		
	6.5.4 Clocks 6.5.5 Counters 6.5.6 Registers 6.5.7 Memories		
6.6	Introduction to Microcomputers		184
	6.6.1 What Are Microcomputers? 6.6.2 Why Use a Microcomputer?		
6.7	Microcomputer Architecture		197
	6.7.1 The Central Processing Unit 6.7.2 Bus Structures 6.7.3 Memory		
	6.7.4 Input-Output Elements and Operations 6.7.5 Hardware and Software 6.7.6 Bit-Slice Architecture		
<b>7.</b>	<b>Grounding and Cabling Techniques</b>		<b>215</b>
7.1	Introduction		215
	7.1.1 Typical Noise Path 7.1.2 Use of Network Theory 7.1.3 Methods of Coupling 7.1.4 Methods of Eliminating Interference 7.1.5 Summary		
7.2	Shielding of Conductors		220
	7.2.1 Capacitive Coupling 7.2.2 Effect of Shield on Capacitive Coupling 7.2.3 Inductive Coupling 7.2.4 Magnetic Coupling between Shield and Inner Conductor 7.2.5 Shielding to Prevent Magnetic Radiation 7.2.6 Shielding a Receiver against Magnetic Fields 7.2.7 Experimental Data 7.2.8 Coaxial Cable Versus Shielded Twisted Pair 7.2.9 Braided Shields 7.2.10 Uniformity of Shield Current 7.2.11 Summary		
7.3	Grounding		241
	7.3.1 Safety Grounds 7.3.2 Signal Grounds 7.3.3 Single-Point Ground Systems 7.3.4 Multipoint Ground Systems 7.3.5 Practical Low-Frequency Grounding 7.3.6 Hardware Grounds 7.3.7 Single Ground Reference for a Circuit 7.3.8 Amplifier Shields 7.3.9 Grounding of Cable Shields 7.3.10 Differential Amplifiers 7.3.11 Shield Grounding at High Frequencies 7.3.12 Guard Shields 7.3.13 Guarded Meters 7.3.14 Cables and Connectors 7.3.15 Summary		

## PART II INSTRUMENTATION

<b>8.</b>	<b>Bridge Transducers</b>		<b>265</b>
8.1	Terminology		265
8.2	Flexural Devices in Measurement Systems		265
	8.2.1 Cantilever Beams 8.2.2 Bourdon Tubes 8.2.3 Clamped Diaphragms 8.2.4 Error Contributions from the Flexure Properties		
8.3	The Resistance Strain Gage		267
	8.3.1 Strain Gage Types and Fabrication 8.3.2 Gage Factor 8.3.3 Mechanical Aspects of Gage Operation 8.3.4 Electrical Aspects of Gage Operation 8.3.5 Technical Societies and Strain Gage Manufacturers		
8.4	The Wheatstone Bridge		276
	8.4.1 Bridge Equations 8.4.2 Lead Wire Effects 8.4.3 Temperature Compensation		

	CONTENTS		ix
8.5	Resistance Bridge Balance Methods		284
8.6	Resistance Bridge Transducer Measurement System Calibration		285
	8.6.1 Static Calibration 8.6.2 Dynamic Calibration 8.6.3 Electrical Substitution Techniques		
8.7	Resistance Bridge Transducer Measurement System Considerations		295
	8.7.1 Bridge Excitation 8.7.2 Signal Amplification 8.7.3 Slip Rings 8.7.4 Noise Considerations		
8.8	AC Impedance Bridge Transducers		303
	8.8.1 Inductive Bridges 8.8.2 Capacitive Bridges		
<b>9.</b>	<b>Position, Velocity, and Acceleration Measurement</b>		<b>307</b>
9.1	Introduction		308
	9.1.1 Terminology 9.1.2 Principles of Transducer Design		
9.2	Position Transducers		310
	9.2.1 Potentiometric and Strain Gage Position Transducers 9.2.2 LVDT and RVDT Transducers and Signal Conditioners 9.2.3 Inductive Proximity Probe Displacement Measurement Systems 9.2.4 Linear and Rotary INDUCTOSYN <sup>®</sup> Position Transducers 9.2.5 Capacitive Position Transducers 9.2.6 Rotary Position Encoders 9.2.7 Ultrasonic Ranging Transducers 9.2.8 Magnetostrictive/Ultrasonic Displacement and Velocity Transducers		
9.3	Solid-State Imagers		350
	9.3.1 Imager Architecture 9.3.2 Array Specifications 9.3.3 Scanning System Considerations		
9.4	Gaging Transducers		359
	9.4.1 Definitions and Scope 9.4.2 Fundamental Characteristics of Gaging Transducers 9.4.3 Electromechanical Gaging Transducers 9.4.4 Pneumatic Gaging Transducers 9.4.5 Nucleonic Gaging Transducers 9.4.6 Infrared and Microwave Gages 9.4.7 Related Technologies		
9.5	Velocity Transducers		366
	9.5.1 Linear Velocity Transducers and Signal Conditioners 9.5.2 Rotary Velocity Transducers 9.5.3 Rotary Velocity Pickups 9.5.4 Seismic Velocity Transducer		
9.6	Acceleration Transducers		378
	9.6.1 Basics of Acceleration Measurement—Seismic Device 9.6.2 Piezoelectric Accelerometer and Its Signal Conditioner 9.6.3 Strain Gage Accelerometer 9.6.4 Capacitive Accelerometers 9.6.5 LVDT Accelerometer 9.6.6 Other Types of Accelerometers		
9.7	Digital Transducers		391
	9.7.1 Transducers with Analog-to-Digital Conversion 9.7.2 Frequency Domain Transducers 9.7.3 Direct Digital Transducers		

x	CONTENTS
9.8	Smart Sensors, Intelligent Transducers and Transmitters 392
	9.8.1 Definition of Smart Sensors, Intelligent Transducers and Transmitters
	9.8.2 Self-Calibration and Diagnostics 9.8.3 Computation
	9.8.4 Communication 9.8.5 Multisensing 9.8.6 Compensation
<b>10.</b>	<b>Force, Torque, and Pressure Measurement 401</b>
10.1	Terminology 401
10.2	Force Transducers and Signal Conditioners 402
	10.2.1 Strain-Gage Load Cell and Its Signal Conditioner
	10.2.2 Piezoelectric Force Transducer and Its Signal Conditioner
	10.2.3 LVDT Load Cell 10.2.4 Capacitive Force Transducer
	10.2.5 Other Types of Load Cells
10.3	Torque Transducers 418
	10.3.1 Rotating vs. Nonrotating Transducers 10.3.2 Strain-Gage Torque
	Transducers 10.3.3 LVDT Torque Transducers 10.3.4 Other Types
	of Torque Transducers
10.4	Pressure Transducers 422
	10.4.1 Basics of Pressure Sensing 10.4.2 Strain-Gage Pressure
	Transducers 10.4.3 Piezoelectric Pressure Transducers
	10.4.4 Capacitive Pressure Transducers 10.4.5 Vibrating Wire
	Pressure Transducer and Its Signal Conditioner 10.4.6 Other
	Types of Pressure Transducers
10.5	Effects of Fluid Transmission Lines in Pressure Measurement 434
	10.5.1 Transfer Function 10.5.2 Capacitance 10.5.3 Frequency
	Response 10.5.4 Example
10.6	Current-Loop Signal Transmission 438
	10.6.1 Background 10.6.2 Current-Loop Concept 10.6.3 Advantages
	and Disadvantages 10.6.4 Types of Transmitters 10.6.5 Using Current
	Transmitters 10.6.6 Electrical Considerations 10.6.7 Current
	Measurements 10.6.8 Practical Example
<b>11.</b>	<b>Temperature and Flow Transducers 445</b>
11.1	Introduction 445
11.2	Thermocouples 446
	11.2.1 Types and Ranges 11.2.2 Peripheral Equipment
	11.2.3 Thermoelectric Theory 11.2.4 Graphical Analysis of Circuits
	11.2.5 Zone-Box Circuits 11.2.6 The Laws of Thermoelectricity
	11.2.7 Switches, Connectors, Zone Boxes, and Reference Baths
	11.2.8 Obtaining High Accuracy with Thermocouples 11.2.9 Service-
	Induced Inhomogeneity Errors 11.2.10 Thermoelectric Materials
	Connected in Parallel 11.2.11 Spurious EMFs Due to Corrosion
	and to Strain
11.3	Resistance Temperature Detectors 461
	11.3.1 Types and Ranges 11.3.2 Physical Characteristics of Typical
	Probes 11.3.3 Electrical Characteristics of Typical Probes
	11.3.4 Thermal Characteristics of Typical Probes 11.3.5 Measuring
	Circuits 11.3.6 The Standard Relationships for Temperature vs. Resistance
	11.3.7 Interpreting Temperature from Resistance: Common Practice

CONTENTS	xi
11.4	Thermistors 467
	11.4.1 Types and Ranges 11.4.2 Physical Characteristics of Typical
	Probes 11.4.3 Electrical Characteristics of Typical Probes
	11.4.4 Thermal Characteristics of Typical Probes 11.4.5 Measuring
	Circuits and Peripheral Equipment 11.4.6 Determining Temperature
	from Resistance
11.5	Fiber-Optic Black-Body Radiation Thermometry 474
	11.5.1 Physical Characteristics 11.5.2 Electrical Characteristics
	11.5.3 Precision and Accuracy 11.5.4 Spatial Resolution
	11.5.5 Temporal Resolution
11.6	Electron Noise Thermometers 476
11.7	Acoustic Velocity Probes 476
11.8	Temperature-Sensitive Coatings 477
11.9	Flow Rate 478
	11.9.1 Nomenclature 11.9.2 Basic Principles Used in Flow
	Measurement 11.9.3 Orifice, Nozzle, and Venturi Meters
	11.9.4 Variable Area Meters 11.9.5 Laminar Flowmeters
	11.9.6 Instability Meters
<b>12.</b>	<b>Signal Processing and Transmission 487</b>
12.1	Passive Signal Processing 487
	12.1.1 Introduction 12.1.2 Low-Pass Filter Functions 12.1.3 Low-
	Pass Filters
12.2	Active Signal Processing 497
	12.2.1 Introduction 12.2.2 RLC Synthesis by Buffer Isolation
	12.2.3 Active Feedback
12.3	Filter Design 503
	12.3.1 Introduction 12.3.2 Scaling Laws and a Design Example
	12.3.3 Transformation Rules, Passive Circuits, 12.3.4 Transformation
	Rules, Active Circuits
12.4	Introduction to Digital Filtering 507
12.5	Implementing Analog Techniques in Digital Formats 507
	12.5.1 Introduction 12.5.2 Review of Analog Filters 12.5.3 Basic
	Design Techniques 12.5.4 Review of Design Assumptions
	12.5.5 Extension of Low-Pass Designs
12.6	Analytic Techniques for Sampled Systems 515
	12.6.1 Introductory Remarks 12.6.2 Sampling 12.6.3 Convolution
	12.6.4 The Z-Transform
12.7	Filter Design Using the Bilinear Transform 519
12.8	Other Types of Digital Filters 520
12.9	Digital Signal Transmission 521
	12.9.1 Characteristics 12.9.2 Advantages Over Analog Signal
	Transmission 12.9.3 Digital Transmission of Analog Signals
	12.9.4 Digital Signal Representation 12.9.5 Digital Signal Encoding
	12.9.6 Digital Signal Error Detection 12.9.7 Digital Signal Media
	12.9.8 Equipment Interfaces for Digital Signal Transmission
	12.9.9 Higher Level Protocols

xii	CONTENTS
<b>13. Data Acquisition and Display Systems</b>	<b>537</b>
13.1 Overview	537
13.2 Data Acquisition	537
13.2.1 Raw Data—Its Acquisition and Conversion	
13.2.2 Engineering Units Conversion	
13.2.3 Data Display	
13.2.4 System Capability	
13.3 Data Acquisition Systems	547
13.3.1 Classes of Systems	
13.3.2 Data Storage Capability	
13.3.3 Displays	
13.3.4 Data Communications	
13.3.5 Data Manipulation Languages	
13.4 Example Systems	557
13.4.1 Hewlett-Packard Model 680	
13.4.2 Micronic M203	
13.4.3 Acurex Autodata Ten/30	
13.4.4 Hewlett-Packard 3045DL with 85F Scientific Computer	
13.4.5 Digital Equipment Company MicroVAX	
13.4.6 Other Approaches	
13.5 Summary	562
 <b>PART III CONTROL</b>	
<b>14. Closed-Loop Control System Analysis</b>	<b>565</b>
14.1 Introduction	565
14.1.1 Closed-Loop versus Open-Loop Control	
14.1.2 Supervisory Control Computers	
14.1.3 Hierarchical Control Computers	
14.1.4 Direct Digital Control (DDC)	
14.1.5 Hybrid Control	
14.1.6 Real Systems with Digital Control	
14.2 Laplace Transforms	568
14.2.1 Single-Sided Laplace Transform	
14.2.2 Transforming LTI Ordinary Differential Equations	
14.2.3 Transfer Function	
14.2.4 Partial Fraction Expansion and Inverse Transform	
14.2.5 Inverse Transform by a General Formula	
14.3 Block Diagrams	576
14.3.1 Block Diagram Reduction	
14.3.2 Transfer Functions of Cascaded Elements	
14.4 $z$ Transforms	579
14.4.1 Single-Sided $z$ Transform	
14.4.2 Poles and Zeroes in the $z$ Plane	
14.4.3 $z$ Transforms of Some Elementary Functions	
14.4.4 Some Important Properties and Theorems of the $z$ Transform	
14.4.5 Pulse Transfer Function	
14.4.6 Zero- and First-Order Hold	
14.5 Closed-Loop Representation	586
14.5.1 Closed-Loop Transfer Function	
14.5.2 Open-Loop Transfer Function	
14.5.3 Characteristic Equation	
14.5.4 Standard Second-Order Transfer Function	
14.5.5 Step Input Response of a Standard Second-Order System	
14.5.6 Effects of an Additional Zero and an Additional Pole	
14.6 Stability	592
14.6.1 Routh-Hurwitz Stability Criterion	
14.6.2 Polar Plots	
14.6.3 Nyquist Stability Criterion	

CONTENTS	xiii
14.7 Steady-State Performance and System Type	602
14.7.1 Step Input	
14.7.2 Ramp Input	
14.7.3 Parabolic Input	
14.7.4 Indices of Performance	
14.7.5 Integral-Square-Error (ISE) Criterion	
14.7.6 Integral of Time-Multiplied Absolute-Error (ITAE) Criterion	
14.7.7 Comparison of Various Error Criteria	
14.8 Simulation for Control System Analysis	608
14.8.1 Analog Computation	
14.8.2 Digital Computation	
14.8.3 Hybrid Computation	
<b>15. Control System Performance Modification</b>	<b>617</b>
15.1 Introduction	617
15.2 Gain and Phase Margin	617
15.2.1 Gain Margin	
15.2.2 Phase Margin	
15.2.3 Gain-Phase Plots	
15.2.4 Polar Plot as a Design Tool in the Frequency Domain	
15.3 Hall Chart	622
15.3.1 Constant-Magnitude Circles	
15.3.2 Constant-Phase Circles	
15.3.3 Closed-Loop Frequency Response for Nonunity Feedback Systems	
15.3.4 Closed-Loop Amplitude Ratio	
15.4 Nichols Chart	626
15.4.1 Closed-Loop Frequency Response from That of Open Loop	
15.4.2 Sensitivity Analysis Using the Nichols Chart	
15.5 Root Locus	629
15.5.1 Angle and Magnitude Conditions	
15.5.2 Time-Domain Design Using the Root Locus	
15.5.3 Time-Domain Response versus $s$ Domain Pole Locations	
15.6 Pole Locations in the $z$ Domain	646
15.6.1 Stability Analysis of Closed-Loop Systems in the $z$ Domain	
15.6.2 Performance Related to Proximity of Closed-Loop Poles to the Unit Circle	
15.6.3 Root Locus in the $z$ Domain	
15.7 Controller Design	649
<b>16. Servoactuators for Closed-Loop Control</b>	<b>651</b>
16.1 Introduction	651
16.1.1 Definitions	
16.1.2 Applications	
16.1.3 Mathematical Models	
16.2 Electrical Servomotors	654
16.3 Direct-Current Servomotors	654
16.3.1 Brushed DC Servomotors	
16.3.2 Brushless DC Servomotors	
16.4 Alternating-Current Servomotors	664
16.4.1 Types of AC Servomotors	
16.4.2 Mathematical Model	
16.5 Stepper Motors	669
16.5.1 Operation	
16.5.2 Types of Stepper Motors	
16.5.3 Mathematical Model of Permanent-Magnet Stepper Motor	
16.5.4 Numerical Example	
16.6 Electrical Modulators	674
16.6.1 Direct-Current Motor Modulators	
16.6.2 Stepper Motor Modulators	

xiv	CONTENTS	
16.7	Hydraulic Servomotors	680
	16.7.1 Linear-Motion Servomotors 16.7.2 Rotary-Motion Servomotors	
	16.7.3 Mathematical Models	
16.8	Hydraulic Modulators	686
	16.8.1 Servovalve Design and Operation 16.8.2 Mathematical Model of a Spool-Type Valve 16.8.3 Mathematical Models for an Electrohydraulic Servovalve	
16.9	Electromechanical and Electrohydraulic Servosystems	695
	16.9.1 Typical Configurations of Electromechanical Servosystems	
	16.9.2 Typical Configurations of Electrohydraulic Servosystems	
	16.9.3 Comparison of Electromechanical and Electrohydraulic Servosystems	
16.10	Steady-State and Dynamic Behavior of Servoactuators and Servosystems	699
	16.10.1 Electromechanical Servoactuators 16.10.2 Electromechanical Servosystems 16.10.3 Electrohydraulic Servoactuators	
	16.10.4 Electrohydraulic Servosystems 16.10.5 Hydraulic Compensation	
	16.10.6 Range of Control for Electrohydraulic and Electromechanical Servosystems	
<b>17.</b>	<b>Controller Design</b>	<b>721</b>
17.1	Introduction	721
17.2	Fundamentals of Closed-Loop Performance	722
	17.2.1 Accuracy and Loop Gain 17.2.2 Dynamic Response and Stability	
17.3	Frequency Compensation to Improve Overall Performance	734
	17.3.1 Well-Damped Systems 17.3.2 Poorly Damped Systems	
	17.3.3 Higher-Order Effects	
17.4	Inner Feedback Loops	743
	17.4.1 Derivatives of the Controlled Variable 17.4.2 Alternative Inner-Loop Variables 17.4.3 Nonelectronic Inner Loops	
17.5	Prefilters and Feed Forward	748
	17.5.1 Lag Prefilters 17.5.2 Lead Prefilters 17.5.3 Feed Forward	
17.6	PID Controllers	753
	17.6.1 Equivalence to Frequency Compensation 17.6.2 Systems Having No Inherent Integration 17.6.3 Systems Having an Inherent Integration	
17.7	Effects of Nonlinearities	761
	17.7.1 Simple Nonlinearities 17.7.2 Complex Nonlinearities	
	17.7.3 Computer Simulation	
17.8	Controller Implementation	764
	17.8.1 Analog Controllers 17.8.2 Hard-Wired Digital Controllers	
	17.8.3 Computer-Based Digital Controllers	

CONTENTS	xv
<b>18. General Purpose Control Devices</b>	<b>773</b>
18.1 Characteristics of General Purpose Control Devices	773
	18.1.1 Hierarchical Control 18.1.2 Programmability 18.1.3 Device Architecture 18.1.4 Sequential Control 18.1.5 Path Control
18.2 Programmable Controllers	780
	18.2.1 Principles of Operation 18.2.2 Interfaces 18.2.3 Programming
18.3 Numerical Controllers	787
	18.3.1 Introduction and Applications 18.3.2 Principles of Operation 18.3.3 Point-to-Point and Contouring Numerical Controllers 18.3.4 NC Programming 18.3.5 Numerical Controllers and CAD/CAM
18.4 Robot Controllers	798
	18.4.1 A Brief History of Industrial Robotics 18.4.2 Elements of a Robot System 18.4.3 Types of Robots 18.4.4 The Structure of a Robot Controller 18.4.5 Programming a Modern Robot Controller
<b>19. State-Space Methods for Dynamic Systems Analysis</b>	<b>807</b>
19.1 Introduction	807
19.2 State-Space Equations for Continuous-Time and Discrete-Time Systems	808
19.3 State-Variable Selection and Canonical Forms	810
	19.3.1 Canonical Forms for Continuous-Time Systems 19.3.2 Canonical Forms for Discrete-Time Systems
19.4 Solution of System Equations	820
	19.4.1 Continuous-Time Systems 19.4.2 Discrete-Time Systems
19.5 Stability	831
19.6 Controllability and Observability	833
19.7 Relationship Between State-Space and Transfer Function Descriptions	838
19.8 Conclusion	840
<b>20. Control System Design Using State-Space Methods</b>	<b>843</b>
20.1 Introduction	843
20.2 The Pole Placement Design Method	843
	20.2.1 Regulation Problem 20.2.2 Modification for Constant Reference and Disturbance Inputs
20.3 The Standard Linear Quadratic Regulator Problem	847
	20.3.1 The Continuous-Time LQR Problem 20.3.2 The Discrete-Time LQR Problem 20.3.3 Stability and Robustness of the Optimal Control Law
20.4 Extensions of the Linear Quadratic Regulator Problem	851
	20.4.1 Disturbance Accommodation 20.4.2 Tracking Applications 20.4.3 Frequency Shaping of Cost Functionals 20.4.4 Robust Servomechanism Control

20.5	Design of Linear State Estimators	858
	20.5.1 The Observer 20.5.2 The Optimal Observer	
20.6	Observer-Based Controllers	865
20.7	Conclusion	869
<b>Index</b>		<b>871</b>