

# Contents

Foreword	xv
Preface	xvii
Acknowledgments	xix
List of Acronyms	xxi
<b>1 Introduction to Microwave Measurements</b>	<b>1</b>
1.1 Modern Measurement Process	2
1.2 A Practical Measurement Focus	3
1.3 Definition of Microwave Parameters	3
1.3.1 <i>S-Parameter Primer</i>	4
1.3.2 <i>Phase Response of Networks</i>	11
1.4 Power Parameters	13
1.4.1 <i>Incident and Reflected Power</i>	13
1.4.2 <i>Available Power</i>	13
1.4.3 <i>Delivered Power</i>	13
1.4.4 <i>Power Available from a Network</i>	14
1.4.5 <i>Available Gain</i>	14
1.5 Noise Figure and Noise Parameters	15
1.5.1 <i>Noise Temperature</i>	16
1.5.2 <i>Effective or Excess Input Noise Temperature</i>	16
1.5.3 <i>Excess Noise Power and Operating Temperature</i>	17
1.5.4 <i>Noise Power Density</i>	17
1.5.5 <i>Noise Parameters</i>	18
1.6 Distortion Parameters	18
1.6.1 <i>Harmonics</i>	19
1.6.2 <i>Second-Order Intercept</i>	19
1.6.3 <i>Two-Tone Intermodulation Distortion</i>	20
1.7 Characteristics of Microwave Components	22
1.8 Passive Microwave Components	23
1.8.1 <i>Cables, Connectors and Transmission Lines</i>	23
1.8.2 <i>Connectors</i>	28
1.8.3 <i>Non-Coaxial Transmission Lines</i>	39
1.9 Filters	42
1.10 Directional Couplers	44

1.11	Circulators and Isolators	46
1.12	Antennas	47
1.13	PCB Components	48
1.13.1	SMT Resistors	48
1.13.2	SMT Capacitors	50
1.13.3	SMT Inductors	51
1.13.4	PCB Vias	52
1.14	Active Microwave Components	52
1.14.1	Linear and Non-Linear	52
1.14.2	Amplifiers: System, Low Noise, High Power	53
1.14.3	Mixers and Frequency Converters	54
1.14.4	Frequency Multipliers and Limiters and Dividers	56
1.14.5	Oscillators	57
1.15	Measurement Instrumentation	57
1.15.1	Power Meters	57
1.15.2	Signal Sources	59
1.15.3	Spectrum Analyzers	60
1.15.4	Vector Signal Analyzers	61
1.15.5	Noise Figure Analyzers	61
1.15.6	Network Analyzers	62
	References	64
<b>2</b>	<b>VNA Measurement Systems</b>	<b>66</b>
2.1	Introduction	66
2.2	VNA Block Diagrams	67
2.2.1	VNA Source	70
2.2.2	Understanding Source Match	72
2.2.3	VNA Test Set	77
2.2.4	Directional Devices	80
2.2.5	VNA Receivers	87
2.2.6	IF and Data Processing	90
2.2.7	Multiport Extensions	92
2.2.8	High Power Test Systems	98
2.3	VNA Measurement of Linear Microwave Parameters	98
2.3.1	Linear Measurements Methods for S-Parameters	99
2.3.2	Power Measurements with a VNA	101
2.3.3	Other Measurement Limitations of the VNA	104
2.3.4	Limitations Due to External Components	107
2.4	Measurements Derived from S-Parameters	108
2.4.1	The Smith Chart	108
2.4.2	Transforming S-Parameters to Other Impedances	114
2.4.3	Concatenating Circuits and T-Parameters	115
2.5	Modeling Circuits Using Y and Z Conversion	117
2.5.1	Reflection Conversion	117
2.5.2	Transmission Conversion	118

2.6	Other Linear Parameters	118
2.6.1	Z-Parameters, or Open-Circuit Impedance Parameters	119
2.6.2	Y-Parameters, or Short-Circuit Admittance Parameters	120
2.6.3	ABCD Parameters	121
2.6.4	H-Parameters or Hybrid Parameters	122
2.6.5	Complex Conversions and Non-Equal Reference Impedances	123
	References	123
<b>3</b>	<b>Calibration and Vector Error Correction</b>	<b>124</b>
3.1	Introduction	124
3.2	Basic Error Correction for S-Parameters: Cal Application	125
3.2.1	Twelve-Term Error Model	126
3.2.2	One-Port Error Model	128
3.2.3	Eight-Term Error Model	128
3.3	Determining Error Terms: Cal Acquisition for 12-Term Models	130
3.3.1	One-Port Error Terms	131
3.3.2	One-Port Standards	132
3.3.3	Two-Port Error Terms	140
3.3.4	Twelve-Term to Eleven-Term Error Model	144
3.4	Determining Error Terms: Cal Acquisition for Eight-Term Models	144
3.4.1	TRL Standards and Raw Measurements	145
3.4.2	Special Cases for TRL Calibration	148
3.4.3	Unknown Thru or SOLR (Reciprocal Thru Calibration)	149
3.4.4	Applications of Unknown Thru Calibrations	151
3.4.5	QSOLT Calibration	153
3.4.6	Electronic Calibration or Automatic Calibration	153
3.5	Waveguide Calibrations	157
3.6	Calibration for Source Power	158
3.7	Calibration for Receiver Power	164
3.7.1	Some Historical Perspective	164
3.7.2	Modern Receiver Power Calibration	165
3.7.3	Response Correction for the Transmission Test Receiver	169
3.8	Devolved Calibrations	172
3.8.1	Response Calibrations	172
3.8.2	Enhanced Response Calibration	174
3.9	Determining Residual Errors	176
3.9.1	Reflection Errors	176
3.9.2	Using Airlines to Determine Residual Errors	178
3.10	Computing Measurement Uncertainties	190
3.10.1	Uncertainty in Reflection Measurements	190
3.10.2	Uncertainty in Source Power	190
3.10.3	Uncertainty in Measuring Power (Receiver Uncertainty)	191
3.11	S21 or Transmission Uncertainty	192
3.12	Errors in Phase	196
3.13	Practical Calibration Limitations	197

3.13.1	<i>Cable Flexure</i>	197
3.13.2	<i>Changing Power after Calibration</i>	198
3.13.3	<i>Compensating for Step Attenuator Changes in Step Attenuators</i>	200
3.13.4	<i>Connector Repeatability</i>	203
3.13.5	<i>Noise Effects</i>	204
3.13.6	<i>Drift: Short-Term and Long-Term</i>	205
3.13.7	<i>Interpolation of Error Terms</i>	206
3.13.8	<i>Calibration Quality: Electronic vs Mechanical Kits</i>	208
	References	210
<b>4</b>	<b>Time Domain Transforms</b>	<b>211</b>
4.1	Introduction	211
4.2	The Fourier Transform	212
4.2.1	<i>The Continuous Fourier Transform</i>	212
4.2.2	<i>Even and Odd Functions and the Fourier Transform</i>	212
4.2.3	<i>Modulation (Shift) Theorem</i>	213
4.3	The Discrete Fourier Transform	214
4.3.1	<i>FFT (Fast Fourier Transform) and IFFT (Inverse Fast Fourier Transform)</i>	214
4.3.2	<i>Discrete Fourier Transforms</i>	216
4.4	Fourier Transform (Analytic) vs VNA Time Domain Transform	216
4.4.1	<i>Defining the Fourier Transform</i>	217
4.4.2	<i>Effects of Discrete Sampling</i>	217
4.4.3	<i>Effects of Truncated Frequency</i>	219
4.4.4	<i>Windowing to Reduce Effects of Truncation</i>	222
4.4.5	<i>Scaling and Renormalization</i>	224
4.5	Low-Pass and Band-Pass Transforms	224
4.5.1	<i>Low-Pass Impulse Mode</i>	224
4.5.2	<i>DC Extrapolation</i>	225
4.5.3	<i>Low-Pass Step Mode</i>	225
4.5.4	<i>Band-Pass Mode</i>	227
4.6	Time Domain Gating	228
4.6.1	<i>Gating Loss and Renormalization</i>	229
4.7	Examples of Time Domain Transforms of Various Networks	232
4.7.1	<i>Time Domain Response of Changes in Line Impedance</i>	232
4.7.2	<i>Time Domain Response of Discrete Discontinuities</i>	233
4.7.3	<i>Time Domain Responses of Various Circuits</i>	233
4.8	The Effects of Masking and Gating on Measurement Accuracy	234
4.8.1	<i>Compensation for Changes in Line Impedance</i>	234
4.8.2	<i>Compensation for Discrete Discontinuities</i>	236
4.8.3	<i>Time Domain Gating</i>	237
4.8.4	<i>Estimating an Uncertainty Due to Masking</i>	241
4.9	Conclusions	241
	References	242

<b>5</b>	<b>Measuring Linear Passive Devices</b>	<b>243</b>
5.1	Transmission Lines, Cables and Connectors	243
5.1.1	<i>Calibration for Low Loss Devices with Connectors</i>	243
5.1.2	<i>Measuring Electrically Long Devices</i>	245
5.1.3	<i>Attenuation Measurements</i>	250
5.1.4	<i>Return Loss Measurements</i>	266
5.1.5	<i>Cable Length and Delay</i>	277
5.2	Filters and Filter Measurements	278
5.2.1	<i>Filter Classes and Difficulties</i>	278
5.2.2	<i>Duplexer and Diplexers</i>	279
5.2.3	<i>Measuring Tunable High-Performance Filters</i>	280
5.2.4	<i>Measuring Transmission Response</i>	282
5.2.5	<i>High Speed vs Dynamic Range</i>	287
5.2.6	<i>Extremely High Dynamic Range Measurements</i>	290
5.2.7	<i>Calibration Considerations</i>	298
5.3	Multiport Devices	299
5.3.1	<i>Differential Cables and Lines</i>	300
5.3.2	<i>Couplers</i>	300
5.3.3	<i>Hybrids, Splitters and Dividers</i>	303
5.3.4	<i>Circulators and Isolators</i>	306
5.4	Resonators	307
5.4.1	<i>Resonator Responses on a Smith Chart</i>	307
5.5	Antenna Measurements	310
5.6	Conclusions	312
	References	313
<b>6</b>	<b>Measuring Amplifiers</b>	<b>314</b>
6.1	Amplifiers as Linear Devices	314
6.1.1	<i>Pretesting an Amplifier</i>	315
6.1.2	<i>Optimizing VNA Settings for Calibration</i>	317
6.1.3	<i>Calibration for Amplifier Measurements</i>	318
6.1.4	<i>Amplifier Measurements</i>	322
6.1.5	<i>Analysis of Amplifier Measurements</i>	328
6.1.6	<i>Saving Amplifier Measurement Results</i>	338
6.2	Gain Compression Measurements	342
6.2.1	<i>Compression Definitions</i>	342
6.2.2	<i>AM-to-PM or Phase Compression</i>	347
6.2.3	<i>Swept Frequency Gain and Phase Compression</i>	348
6.2.4	<i>Gain Compression Application, Smart Sweep and Safe-Sweep Mode</i>	349
6.3	Measuring High-Gain Amplifiers	354
6.3.2	<i>Calibration Considerations</i>	357
6.4	Measuring High-Power Amplifiers	359
6.4.1	<i>Configurations for Generating High Drive Power</i>	360
6.4.2	<i>Configurations for Receiving High Power</i>	362
6.4.3	<i>Power Calibration and Pre/Post Leveling</i>	364

6.5	Making Pulsed-RF Measurements	365
6.5.2	<i>Pulse Profile Measurements</i>	369
6.5.3	<i>Pulse-to-Pulse Measurements</i>	371
6.5.4	<i>DC Measurements for Pulsed RF Stimulus</i>	372
6.6	Distortion Measurements	374
6.6.1	<i>Harmonic Measurements on Amplifiers</i>	374
6.6.2	<i>Two-Tone Measurements, IMD and TOI Definition</i>	378
6.6.3	<i>Measurement Techniques for Two-Tone TOI</i>	382
6.6.4	<i>Swept IMD</i>	382
6.6.5	<i>Optimizing Results</i>	385
6.6.6	<i>Error Correction</i>	390
6.7	Noise Figure Measurements	391
6.7.1	<i>Definition of Noise Figure</i>	391
6.7.2	<i>Noise Power Measurements</i>	392
6.7.3	<i>Computing Noise Figure from Noise Powers</i>	394
6.7.4	<i>Computing DUT Noise Figure from Y-Factor Measurements</i>	395
6.7.5	<i>Cold-Source Methods</i>	397
6.7.6	<i>Noise Parameters</i>	399
6.7.7	<i>Error Correction in Noise Figure Measurements</i>	402
6.7.8	<i>Uncertainty of Noise Figure Measurements</i>	404
6.7.9	<i>Verifying Noise Figure Measurements</i>	405
6.7.10	<i>Techniques for Improving Noise Figure Measurements</i>	406
6.8	X-Parameters, Load Pull Measurements and Active Loads	408
6.8.1	<i>Non-Linear Responses and X-Parameters</i>	408
6.8.2	<i>Load Pull, Source-Pull and Load Contours</i>	411
6.9	Conclusions on Amplifier Measurements	416
	References	417
<b>7</b>	<b>Mixer and Frequency Converter Measurements</b>	<b>418</b>
7.1	Mixer Characteristics	418
7.1.1	<i>Small Signal Model of Mixers</i>	421
7.1.2	<i>Reciprocity in Mixers</i>	425
7.1.3	<i>Scalar and Vector Responses</i>	427
7.2	Mixers vs Frequency Converters	427
7.2.1	<i>Frequency Converter Design</i>	428
7.2.2	<i>Multiple Conversions and Spur Avoidance</i>	429
7.3	Mixers as a 12-Port Device	430
7.3.1	<i>Mixer Conversion Terms</i>	431
7.4	Mixer Measurements: Frequency Response	434
7.4.1	<i>Introduction</i>	434
7.4.2	<i>Amplitude Response</i>	434
7.4.3	<i>Phase Response</i>	437
7.4.4	<i>Group Delay and Modulation Methods</i>	448
7.4.5	<i>Swept LO Measurements</i>	451

7.5	Calibration for Mixer Measurements	455
7.5.1	<i>Calibrating for Power</i>	455
7.5.2	<i>Calibrating for Phase</i>	457
7.5.3	<i>Determining the Phase and Delay of a Reciprocal Calibration-Mixer</i>	460
7.6	Mixers Measurements vs Drive Power	472
7.6.1	<i>Mixer Measurements vs LO Drive</i>	472
7.6.2	<i>Mixer Measurements vs RF Drive Level</i>	476
7.7	TOI and Mixers	480
7.7.1	<i>IMD vs LO Drive Power</i>	481
7.7.2	<i>IMD vs RF Power</i>	481
7.7.3	<i>IMD vs Frequency Response</i>	484
7.8	Noise Figure in Mixers and Converters	486
7.8.1	<i>Y-Factor Measurements on Mixers</i>	486
7.8.2	<i>Cold Source Measurements on Mixers</i>	488
7.9	Special Cases	494
7.9.1	<i>Mixers with RF or LO Multipliers</i>	494
7.9.2	<i>Segmented Sweeps</i>	495
7.9.3	<i>Measuring Higher-Order Products</i>	496
7.9.4	<i>Mixers with an Embedded LO</i>	500
7.9.5	<i>High-Gain and High-Power Converters</i>	503
7.10	Conclusions on Mixer Measurements	504
	References	505
<b>8</b>	<b>VNA Balanced Measurements</b>	<b>506</b>
8.1	Four-Port Differential and Balanced S-Parameters	506
8.2	Three-Port Balanced Devices	511
8.3	Measurement Examples for Mixed Mode Devices	512
8.3.1	<i>Passive Differential Devices: Balanced Transmission Lines</i>	512
8.3.2	<i>Differential Amplifier Measurements</i>	516
8.3.3	<i>Differential Amplifiers and Non-Linear Operation</i>	519
8.4	True Mode VNA for Non-Linear Testing	523
8.4.1	<i>True Mode Measurements</i>	526
8.4.2	<i>Determining the Phase-Skew of a Differential Device</i>	531
8.5	Differential Testing Using Baluns, Hybrids and Transformers	533
8.5.1	<i>Transformers vs Hybrids</i>	533
8.5.2	<i>Using Hybrids and Baluns with a Two-Port VNA</i>	537
8.6	Distortion Measurements of Differential Devices	539
8.6.1	<i>Comparing Single Ended IMD Measurement to True Mode Measurements</i>	541
8.7	Noise Figure Measurements on Differential Devices	544
8.7.1	<i>Mixed Mode Noise Figure</i>	545
8.7.2	<i>Measurement Setup</i>	546
8.8	Conclusions on Differential Device Measurement	550
	References	550

---

<b>9</b>	<b>Advanced Measurement Techniques</b>	<b>552</b>
9.1	Creating Your Own Cal Kits	552
	9.1.1 <i>PCB Example</i>	553
	9.1.2 <i>Evaluating PCB Fixtures</i>	554
9.2	Fixturing and De-embedding	569
	9.2.1 <i>De-embedding Mathematics</i>	570
9.3	Determining S-Parameters for Fixtures	572
	9.3.1 <i>Fixture Characterization Using One-Port Calibrations</i>	573
9.4	Automatic Port Extensions	578
9.5	AFR: Fixture Removal Using Time Domain	583
9.6	Embedding Port-Matching Elements	588
9.7	Impedance Transformations	591
9.8	De-embedding High-Loss Devices	592
9.9	Understanding System Stability	595
	9.9.1 <i>Determining Cable Transmission Stability</i>	595
	9.9.2 <i>Determining Cable Mismatch Stability</i>	596
	9.9.3 <i>Reflection Tracking Stability</i>	597
9.10	Some Final Comments on Advanced Techniques and Measurements	598
	References	599
<b>Appendix A</b>	<b>Physical Constants</b>	<b>600</b>
<b>Appendix B</b>	<b>Common RF and Microwave Connectors</b>	<b>601</b>
<b>Appendix C</b>	<b>Common Waveguides</b>	<b>602</b>
<b>Appendix D</b>	<b>Some Definitions for Calibration Kit Open and Shorts</b>	<b>603</b>
<b>Index</b>		<b>606</b>