

CONTENTS

1 BASIC CONCEPTS, 1

Questions and Problems, 4

2 TRANSMISSION LINES, 5

2.1. Types of Transmission Lines, 6 2.2. Losses, 7 2.3. The Infinite Line, 9 2.4. Attenuation, 10 2.5. Phase, 11 2.6. Characteristic Impedance, 12 2.7. Reflection Coefficient, 13 2.8. Standing Waves, 15 2.9. Total Reflection, 15 2.10. Partial Reflection, 16 2.11. Standing-Wave Ratio, 17 2.12. Power, 18 2.13. Impedance, 19 2.14. Examples, 22 2.15. The Smith Chart, 23 2.16. Smith Chart Solutions to Problems, 26 2.17. Reactive Stubs, 27 2.18. Double-Stub Tuner, 28 2.19. Baluns, 29 2.20. Multiple Reflections, 30 Questions and Problems, 31

3 MICROWAVE MEASUREMENTS, 33

3.1. Detectors, 34 3.2. High-Power Measurements, 35 3.3. Low-Power Measurements, 37 3.4. Attenuation, 38 3.5. VSWR, 40 3.6. **Reflectorimeter**, 42 3.7. Impedance, 43 3.8. Frequency, 46 3.9. Phase, 47 3.10. Sweep Oscillators, 50 Questions and Problems, 54

4 WAVEGUIDES, 56

4.1. Modes, 57 4.2. Cut-Off Wavelength, 60 4.3. Guide **Wavelength**, 61 4.4. Phase Velocity and Group Velocity, 62 4.5. Choice of Dimensions, 63 4.6. Impedance, 63 4.7. Dielectric, 64 4.8. Discontinuities, 65 4.9. Bends, Corners, and Twists, 68 4.10. Mode Filters, 69 4.11. Power Handling Capability, 70 4.12. Attenuation, 71 4.13. Materials, 72 4.14. Flanges, 73 4.15. Ridge Waveguide, 74 Questions and Problems, 75

5 COAXIAL LINES, 77

5.1. Modes, 77 5.2. Characteristic Impedance, 79 5.3. Phase Velocity, 79 5.4. Attenuation, 80 5.5. Voltage Breakdown and Maximum Power, 81

5.6. Fixed Frequency, 81 5.7. Choice of Dimensions, 82 5.8. Stub Supports, 82 5.9. Beads, 84 5.10. Cables, 85 5.11. Discontinuities, 85 5.12. Corners, 87 5.13. Other TEM Lines, 87 Questions and Problems, 87

6 METHODS OF MATCHING, **89**

6.1. Quarter-Wave Transformers, 89 6.2. Half-Wave Transformers, 94 6.3. Tapers, 95 6.4. Short Transformers, 95 6.5. Shunt Discontinuities, 98 6.6. Choice of Matching, 100 6.7. Examples, 100 6.8. Empirical Matching, 107 Questions and Problems, 108

7 TEES AND COUPLERS, **110**

7.1. Waveguide H-Plane Tee, 110 7.2. Waveguide E-Plane Tee, 113 7.3. Bifurcated Waveguide, 113 7.4. Magic Tee, 115 7.5. Coaxial Tee, 117 7.6. Directional Coupler, 119 7.7. Hybrids, 123 Questions and Problems, 127

8 MICROWAVE COMPONENTS, **129**

8.1. Matched Loads, 129 8.2. Fixed Attenuators, 132 8.3. Variable Attenuators, 132 8.4. Cut-Off Attenuator, 134 8.5. Variable **Phase**-Shifters, 135 8.6. Transitions, 136 8.7. Waveguide-To-Coax Transitions, 138 8.8. Crystal and Bolometer Holders, 140 8.9. Rotary Joints, 141 8.10. Ferrite Components, 142 8.11. Fixed Mismatch, 142 Questions and Problems, 143

9 RESONANT CAVITIES AND FILTERS, **145**

9.1. Resonant Cavity, 146 9.2. Modes in Cavities, 146 9.3. Resonant Frequency, 147 9.4. Quarter-Wave Cavity, 150 9.5. Coupling, 151 9.6. Q-Factor, 153 9.7. Cavity Measurements, 154 9.8. Applications of Cavities, 155 9.9. Filters, 157 9.10. Band-Pass Filter, 158 9.11. **Low**-Pass Filter, 158 9.12. High-Pass Filter, 159 9.13. Band-Stop Filter, 159 9.14. Filter Measurements, 159 9.15. Applications of Filters, 160 Questions and Problems, 161

10 MIXERS AND DETECTORS, **163**

10.1. Physical Design, 163 10.2. Equivalent Circuit, 165 10.3. Detector Crystals, 166 10.4. Video Impedance of Detectors, 167 10.5. D-C Bias, 167 10.6. Sensitivity of Detectors, 167 10.7. Mixers, 170 10.8. Mixer Sensitivity and Noise, 171 10.9. Effect of r-f Amplifier on Noise Figure,

172 10.10. Noise Figure Measurements, 173 10.11. Balanced Mixers, 175
10.12. Power Considerations, 176 10.13. Other Diodes, 176 Questions
and Problems, 177

11 SWITCHING, 179

11.1. Mechanical Switches, 179 11.2. Diode Switches, 183 11.3. Ferrite
Switches, 184 11.4. Gas Switches, 185 11.5. Measurements, 186 11.6.
Power Handling Capability, 189 11.7. Control Power, 190 11.8. Du-
plexers, 190 11.9. Ferrite Duplexers, 193 11.10. Crystal Protection, 194
11.11. Diplexers, 195 11.12. Modulators, 196 Questions and Problems,
197

12 ANTENNAS, 199

12.1. Reciprocity, 199 12.2. Gain, 200 12.3. Polarization, **200** 12.4.
Beam Pattern, 202 12.5. Sidelobes, 204 12.6. Beamwidth, 205 12.7.
Antenna Types, 206 12.8. Conical Scanning, 207 12.9. Monopulse, 208
12.10. Sequential **Lobing**, 208 12.11. Near and Far Zones, 210 12.12.
Frequency, 211 12.13. r-f Dark Room, 211 12.14. VSWR Measure-
ments, 212 12.15. Gain Measurements, 212 12.16. Primary Gain Stand-
ard, 214 12.17. Pattern Measurements, 215 Questions and Problems, 216

13 MICROWAVE TUBES, 218

13.1. Disk-Seal Triodes, 218 13.2. Interaction, 220 13.3. Feedback, 221
13.4. Velocity Modulation, 222 13.5. Multicavity Klystron, 223 13.6.
Reflex Klystron, 224 13.7. Magnetron, 225 13.8. Frequency Consider-
ations, 228 13.9. Traveling-Wave Tube, 231 13.10. Backward Wave
Oscillator, 232 13.11. Spurious Signals, 233 13.12. Other Tubes, 234
Problems and Questions, 234

APPENDIX, **236**

INDEX, **239**